



## [Implement a clip-detection circuit for BTL Class D amplifiers](#)

[Dimitri Danyuk](#) - March 05, 2009

Clip detection is a convenient feature in Class AB amplifiers. It produces a signal from a clip-detection pin that drives an automatic volume control, which reduces gain compression and distortion when the amplifier is overdriven. Class AB amplifiers, such as the [STMicroelectronics](#) TDA7293, TDA7396, STA7360, and STA540 and the [Toshiba](#) TA8275 and TB29xx, have on-chip clip-detection circuits. Newer Class D automotive amplifiers, such as the four-channel STMicroelectronics TDA7454 and the [Texas Instruments](#) TAS5414/5424, have on-chip clip-detection circuits, but these ICs use a common clip-detection pin, comprising hardware ORed inside the IC, for all four channels. Other Class D amplifiers lack the clip-detection feature altogether, but you can implement it with external components.

An analog-input Class D amplifier comprises PWM (pulse-width-modulation) logic, gate-drive circuits, and a power stage. The PWM logic transforms the analog-input signal into a PWM signal. The power stage with the gate drivers transforms the low-power PWM signal into a high-voltage, high-current PWM sequence. A BTL (bridge-tied-load) amplifier basically comprises two gate-drive circuits and two power stages, which the same PWM signal drives. The signal directly drives one gate-drive circuit and phase-inverts the other. In theory, a BTL amplifier can produce four times more power into the same load than a single-ended amplifier.

[Figure 1](#) illustrates the implementation of an external clip-detection circuit to a BTL-Class D-amplifier IC. The voltage swing on each output is symmetrical and is within the range of voltage drop on the on-resistance of MOSFET  $Q_6$  to the common-collector voltage,  $V_{CC}$ , minus the voltage drop on the on-resistance of MOSFET  $Q_3$ . When the output voltage reaches a certain threshold,  $Q_1$  turns off. The component values of  $R_1$ ,  $R_2$ , and  $R_3$  and the voltage drop across diodes  $D_1$  through  $D_4$  set this threshold, which is 0.5V with respect to power ground,  $P_{GND}$ , for the given component values. A positive-going pulse appears on the collector of  $Q_1$  whenever the output voltage is below the threshold with respect to power ground. This pulse alerts the host microcontroller to the existence of clipping ([Figure 2](#)). Capacitor  $C_1$  filters the residual of the switching- and high-frequency content of the audio signal.

A simple application involves filtering and integrating the pulses with further automatic reduction and restoration of the volume setting using the microcontroller's driven-volume control to counteract the clipping distortion. You can also implement more sophisticated algorithms ([Reference 1](#)). A suitable peak detector comprising  $Q_2$ ,  $R_5$ , and  $C_2$  allows the circuit to hold the short clipping pulses for a longer time. You can add LED circuitry to provide a visual clipping indication.

### Reference

1. Person, Andrew P, and James P Muccioli, "[Adjustable Clip Detection System](#)," US Patent, 5,453,716, Sept 26, 1995, US Patent Office.

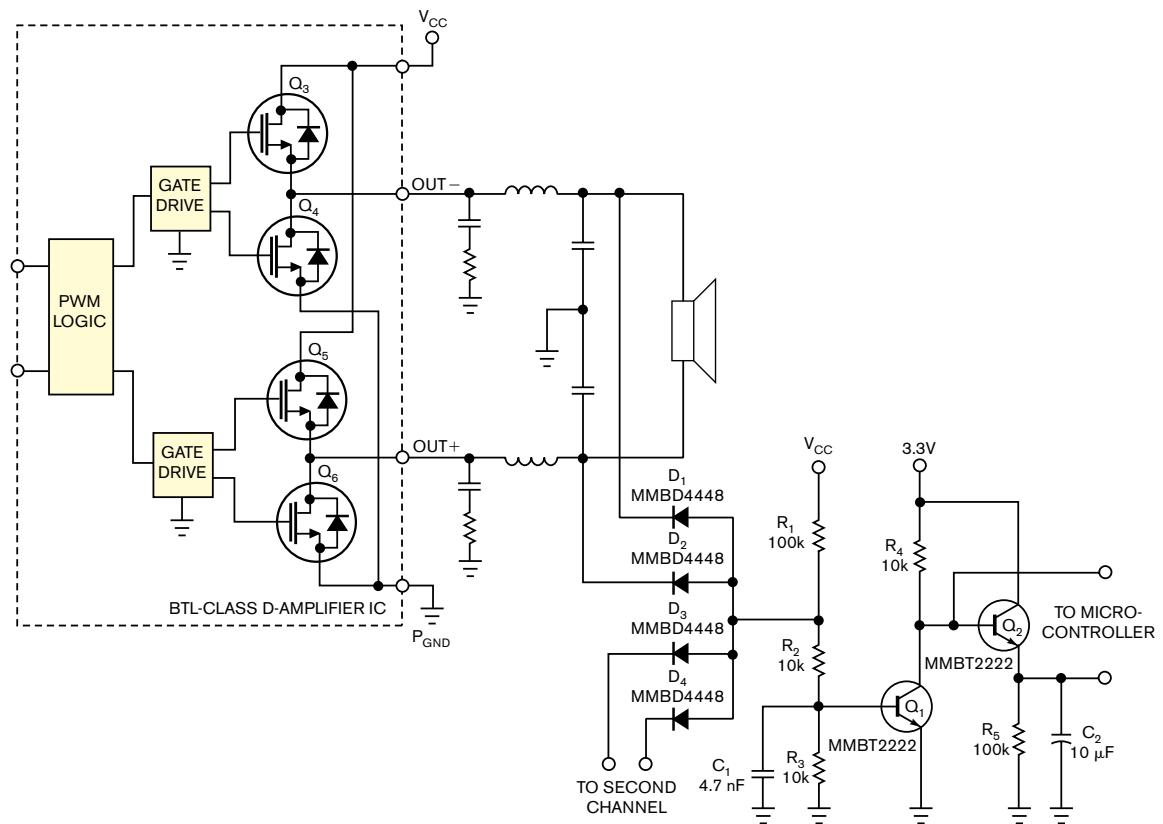


Figure 1 Adding several components to the BTL-Class D-amplifier IC provides a clip-detection function. A peak detector, comprising Q<sub>2</sub>, R<sub>5</sub>, and C<sub>2</sub>, is optional.

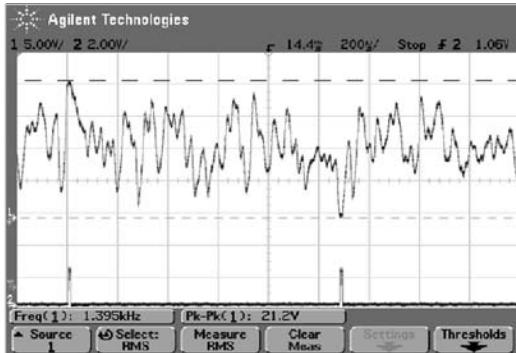


Figure 2 A positive-going pulse appears on the collector of  $Q_1$  whenever the output voltage is below the threshold with respect to power ground.