

REGULARS

CIRCUIT IDEAS

D. Danyuk, G. Pilko. // Accurate Astable Multivibrator Timing. // Electronics World + Wireless World. 1992. January. P. 58.

Four channels on a single-channel oscilloscope

On a single-channel oscilloscope, this circuit, using only four ICs, multiplexes four signal channels for, effectively, simultaneous display.


The differential 4052 multiplexer works with two sets of four inputs: pins 11, 12, 14 and 15 carry the y signal, while pins 1, 2, 4 and 5 take DC potentials from the four potentiometers to determine the y position on the screen (a DC-coupled oscilloscope is assumed).

Clock pulses variable up to 2MHz are generated by the 4047 astable and drive the 2-bit Johnson counter, which produces A and B select waveforms for the multiplexer. High switching rates multiplex the y inputs at a higher rate than the oscilloscope sweep to give a virtually continuous display.

Output to the single input of the oscilloscope comes from an LM318 variable-gain op-amp.

V Lakshminarayanan

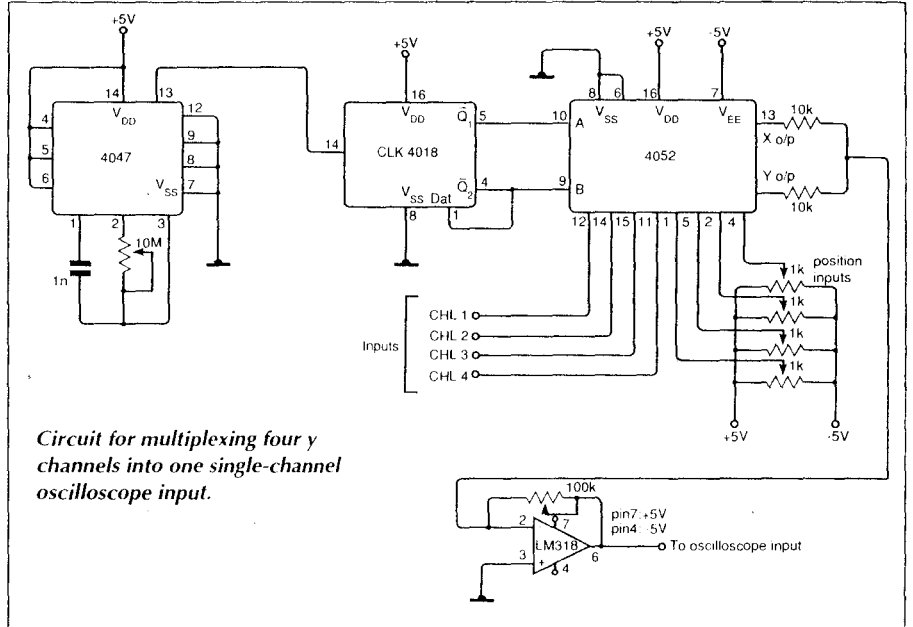Centre for Development of Telematics
Bangalore, India



Accurate astable multivibrator timing

In the free-running multivibrator of Fig. 1 the period is theoretically given by $T = 2CR_1 \ln(1 + 2R_2/R_3)$, positive and negative excursions being exactly equal.

Symmetry of the output waveform suffers in practice when the differential input voltage exceeds the specified value and, in some types of op-amp, causes an avalanche input current. This usually happens as a

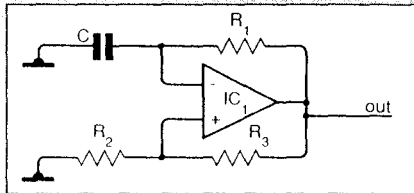


Fig. 1. Commonly used multivibrator circuit may give asymmetrical output if inverting input avalanches.

result of exceeding input threshold protection or when long-tailed pair base/emitter zener action occurs.

Figure 2 shows an improved circuit, in which the unity-gain buffer IC₂ isolates the timing circuit from the inverting input of

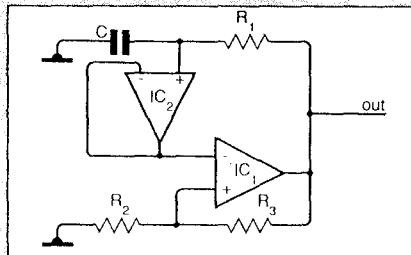


Fig. 2. Modified circuit isolates timing components from inverting input to preserve symmetry.

IC₁, incidentally affording increased speed. Alternatively, the potential divider R_{2,3} may be varied to give a lower differential input swing, but in this case the op-amp offset voltage cannot be neglected.

Dmitri Danyuk and George Pilko
Kiev, USSR

FRESH IDEAS

While we are not short of Circuit Ideas to publish, it would be agreeable to see some fresh input from the vast, untapped bank of talent that our thousands of readers represent. We pay a moderate fee for all ideas published. So send them to Circuit Ideas, EW+WW, Room L333, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS. We will be happy to consider them.