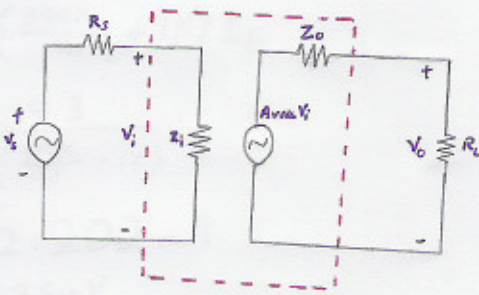


Year 2005/2006 S2

EG2002

Qn:1)

(a)



$$\begin{aligned} Z_i &= 1.2 \text{ k}\Omega \\ R_s &= 100 \Omega \\ A_{VNL} &= -125 \\ Z_o &= 2.4 \text{ k}\Omega \\ R_L &= 3.3 \text{ k}\Omega \end{aligned}$$

(f)

$$\begin{aligned} R_s &= 0 \Omega \# \\ R_L &= \infty \Omega \# \end{aligned}$$

$R_s$  is short circuit,  $R_L$  is open circuit.

(g)

$$V_o = V_i A_{VNL}$$

$$V_s = V_i$$

$$\begin{aligned} \therefore A_{VL} &= \frac{V_i A_{VNL}}{V_i} \\ &= A_{VNL} \\ &= -125 \# \end{aligned}$$

$$(b) V_i = \left( \frac{Z_i}{Z_i + R_s} \right) V_s$$

$$\frac{V_i}{V_s} = \frac{Z_i}{Z_i + R_s} \#$$

$$(c) V_o = \left( \frac{R_L}{R_L + Z_o} \right) \times A_{VNL} V_i$$

$$\frac{V_o}{V_i} = -125 \left( \frac{R_L}{R_L + Z_o} \right) \#$$

$$(d) V_s = \left( \frac{Z_i + R_s}{Z_i} \right) V_i$$

$$V_o = -125 \left( \frac{R_L}{R_L + Z_o} \right) V_i$$

$$A_{Vs} = \frac{V_o}{V_s}$$

$$= \frac{-125 \left( \frac{R_L}{R_L + Z_o} \right) V_i}{\left( \frac{Z_i + R_s}{Z_i} \right) V_i}$$

$$= -125 \left[ \frac{R_L Z_i}{(Z_i + R_s)(R_L + Z_o)} \right] \#$$

$$(e) A_{Vs} = -125 \left[ \frac{(3.3 \text{ k}\Omega)(1.2 \text{ k}\Omega)}{(1.2 \text{ k}\Omega + 100 \Omega)(3.3 \text{ k}\Omega + 2.4 \text{ k}\Omega)} \right]$$

$$= -125 \left[ \frac{3.96 \text{ M}\Omega}{(1.3 \text{ k}\Omega)(5.7 \text{ k}\Omega)} \right]$$

$$= -125 (0.5344)$$

$$= -66.80 \#$$

Qn.2)

$$(a) V_{CC} = I_B R_B + V_{BE} + I_E R_E$$

$$10 - 0.7 = \left( \frac{I_E}{1+120} \right) (390K) + I_E (1K\Omega)$$

$$9.3 = \left( \frac{390K}{121} + 1K \right) I_E$$


$$I_E = \frac{9.3}{\left( \frac{390K}{121} + 1K \right)}$$

$$= 2.202 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{2.202 \text{ mA}}$$

$$= 11.81 \Omega \#$$

(b)

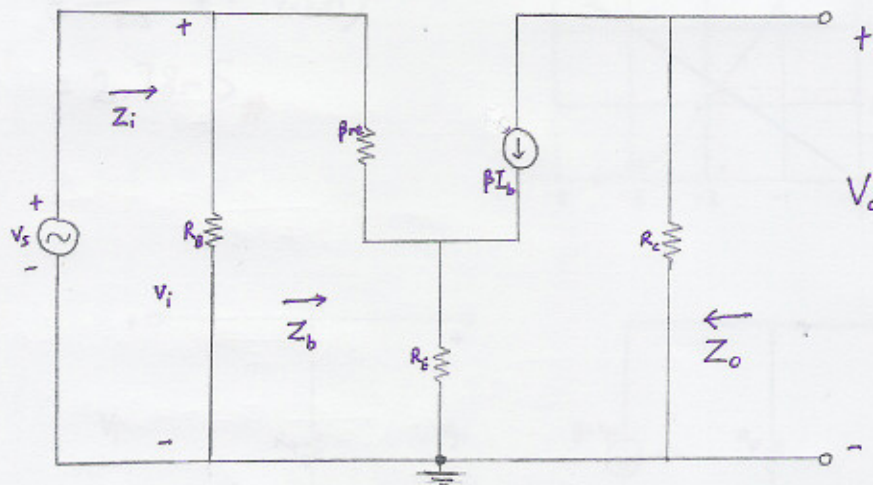

$$\beta = 120$$

$$R_B = 390K\Omega$$

$$R_E = 1K\Omega$$

$$R_C = 3.3K\Omega$$

$$\beta r_e = (120)(11.81)$$

$$= 1.4172K\Omega$$

$$(c) Z_i = R_B \parallel Z_b$$

$$Z_b = \beta r_e + (1+\beta)R_E$$

$$= 1.4172K\Omega + (1+120)(1K\Omega)$$

$$= 122.417K\Omega$$

$$\therefore Z_i = (390K\Omega) \parallel (122.417K\Omega)$$

$$= 93.171K\Omega \#$$

$$Z_o = R_C$$

$$= 3.3K\Omega \#$$

$$(d) V_o = -\beta I_b R_C$$

$$V_i = I_b \beta (r_e + R_E)$$

$$\therefore A_{v_{mid}} = - \frac{\beta I_b R_C}{I_b \beta (r_e + R_E)}$$

$$= \frac{-3.3K\Omega}{(11.81\Omega + 1K\Omega)}$$

$$= -3.26 \#$$

$$(e) R_{CC} = R_C + R_L$$

$$= 3.3K\Omega + \infty\Omega$$

$$= \infty\Omega$$

$$\therefore f_{LC} = \frac{1}{2\pi R_{CC} C_C}$$

$$= \frac{1}{2\pi (\infty) (0.47\mu F)}$$

$$= 0 \text{ Hz} \#$$



Qn:3)

(a) Self-biasing & Common Source.

$$(b) I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$I_D = (10\text{mA}) \left(1 - \frac{V_{GS}}{(-3.5)}\right)^2$$

$$I_D = -\frac{V_{GS}}{R_S}$$


$$I_D = -\frac{V_{GS}}{750\Omega}$$

$V_{GS}$	0	-1.5	-2.5	-3.5	} curve
$I_D$	10	3.27	0.81	0	
$V_{GS}$	0	-3.5	} Line		
$I_D$	0	4.67			

$$g_m = \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GSQ}}{V_P}\right)$$

$$= \frac{2(10\text{mA})}{3.5} \left(1 - \frac{(-1.8)}{(-3.5)}\right)$$


$$= 2.78\text{mS} \#$$

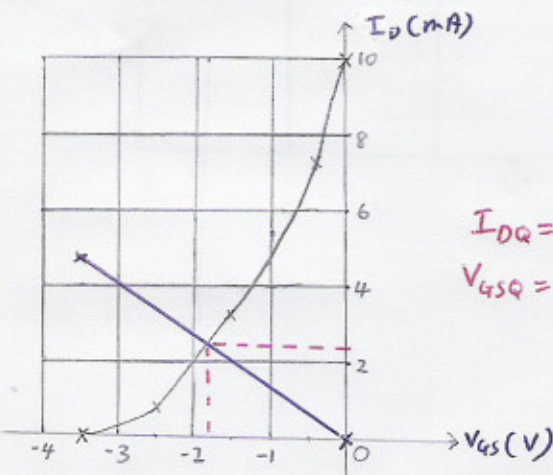

$$I_{DQ} = 2.4\text{mA}$$

$$V_{GSQ} = -1.8\text{V}$$

(c)

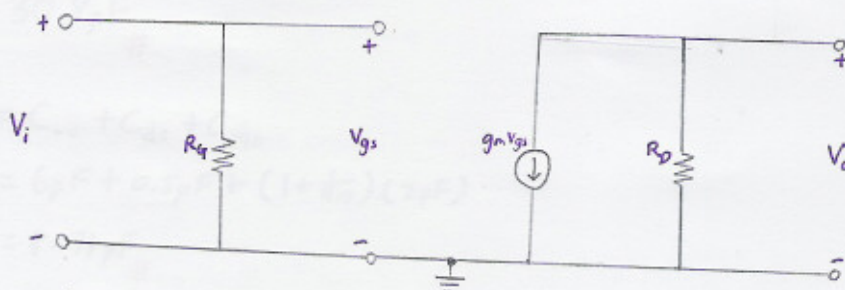

$$I_{DSS} = 10\text{mA}$$

$$V_P = -3.5\text{V}$$

$$R_G = 10\text{M}\Omega$$

$$R_D = 1.5\text{K}\Omega$$

$$V_o = (-g_m V_{GS})(R_D)$$

$$V_i = V_{GS}$$

$$A_v = \frac{V_o}{V_i}$$

$$= -g_m R_D$$

$$= -2.78\text{mS}(1.5\text{K}\Omega)$$

$$= -4.17 \#$$

(d)

$$V_o = -g_m V_{GS} R_D$$

$$V_i = V_{GS} + g_m V_{GS} R_S$$

$$= V_{GS}(1 + g_m R_S)$$

$$A_v = \frac{V_o}{V_i}$$

$$= \frac{-g_m R_D}{1 + g_m R_S}$$

$$= -1.35 \#$$

(a) Fixed Biasing

$$(b) V_o = -g_m V_{gs} R_D$$

$$V_i = V_{gs}$$

$$A_v = \frac{V_o}{V_i}$$


$$= -g_m R_D$$

$$= -(2 \text{ mS})(4.7 \text{ k}\Omega)$$

$$= -9.4$$

$$A_v(\text{dB}) = 20 \lg 9.4$$

$$= 19.46 \text{ dB} \#$$

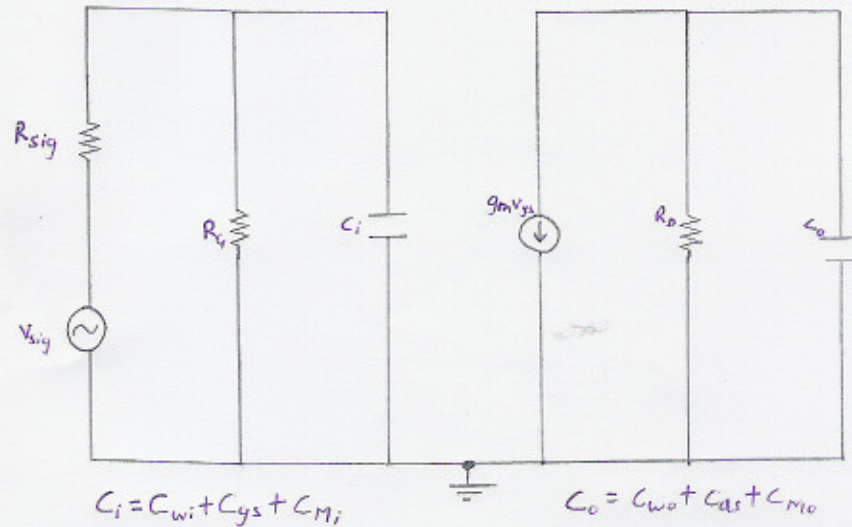

(c) (i)

$$C_i = C_{wi} + C_{gs} + C_{M_i}$$

$$= 5 \text{ pF} + 5 \text{ pF} + (1 - A_v) C_{gd}$$

$$= 10 \text{ pF} + (1 + 9.4)(2 \text{ pF})$$

$$= 30.8 \text{ pF} \#$$

(ii)  $C_o = C_{wo} + C_{ds} + C_{M_o}$

$$= 6 \text{ pF} + 0.5 \text{ pF} + (1 + \frac{1}{9.4})(2 \text{ pF})$$

$$= 8.71 \text{ pF} \#$$

(d)  $F_{Hi} = \frac{1}{2\pi (R_{sig} \parallel R_g) (C_i)}$

$$= \frac{1}{2\pi (10 \text{ k}\Omega \parallel 1 \text{ M}\Omega) (30.8 \text{ pF})}$$

$$= 521.96 \text{ kHz}$$


$$F_{Ho} = \frac{1}{2\pi (R_D) (C_o)}$$

$$= \frac{1}{2\pi (4.7 \text{ k}\Omega) (8.71 \text{ pF})}$$

$$= 3.887 \text{ MHz}$$

$$\therefore f_H = 521.96 \text{ kHz} \#$$

(e) Gain (dB)

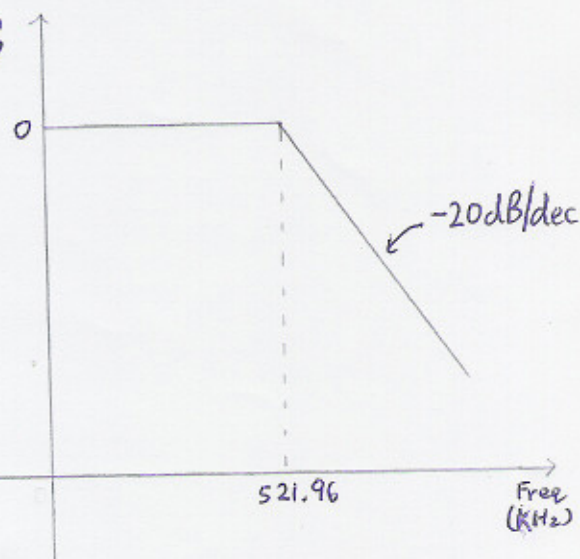



Qn: 5)

(a) (i) Both  $Q_1$  and  $Q_2$  are self-biasing and Common Source Amplifier #

(ii)  $V_{in1} = V_{gs1}$

$$V_{out1} = -g_m V_{gs1} (R_{D1} \parallel R_{G2})$$

$$\begin{aligned} A_{v1} &= \frac{V_{out1}}{V_{in1}} \\ &= -g_m (R_{D1} \parallel R_{G2}) \\ &= -2.51 \text{ mS} (2.2 \text{ k} \parallel 10 \text{ M}) \\ &= -5.52 \# \end{aligned}$$

$$V_{in2} = V_{gs2}$$

$$V_{out2} = -g_m V_{gs2} (R_{D2} \parallel R_L)$$

$$\begin{aligned} A_{v2} &= \frac{V_{out2}}{V_{in2}} \\ &= -g_m (R_{D2} \parallel R_L) \\ &= -2.51 \text{ mS} (2.2 \text{ k} \parallel 2.2 \text{ k}) \\ &= -2.76 \# \end{aligned}$$

(iii)  $\frac{V_o}{V_s} = A_{v1} \times A_{v2}$

$$\begin{aligned} &= -5.52 \times -2.76 \\ &= 15.24 \# \quad (V_s = V_i, \text{ cause no } R_s) \end{aligned}$$

(b)  $I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta_D R_E}$

$$\begin{aligned} &= \frac{16 - 1.4 \text{ V}}{2.4 \text{ M}\Omega + 8000 (510)} \\ &= \frac{14.6 \text{ V}}{6.48 \text{ M}\Omega} \\ &= 2.25 \mu\text{A} \end{aligned}$$

$$\begin{aligned} I_E &= (1 + \beta_D) I_B \\ &= (1 + 8000) (2.25 \mu\text{A}) \\ &= 18.03 \text{ mA} \# \end{aligned}$$

Qn: 6)

$$\begin{aligned} \text{(a) (i)} \quad A_{CL} &= -\frac{R_f}{R_i} \\ &= -\frac{200\text{k}\Omega}{1\text{k}\Omega} \\ &= -200 \# \end{aligned}$$

$$\begin{aligned} \text{(ii)} \quad Z_i &= R_i \\ &= 1\text{k}\Omega \# \end{aligned}$$

$$\begin{aligned} \text{(iii)} \quad Z_o &= Z_{o(\text{op-amp})} \\ &= 60\Omega \# \end{aligned}$$

$$\begin{aligned} \text{(iv)} \quad \text{CMRR} &= \left| \frac{A_{CL}}{A_{CM}} \right| \\ &= \left| \frac{-200}{0.002} \right| \\ &= |-100\text{k}| \\ &= 100 \times 10^3 \# \end{aligned}$$

$$\begin{aligned} \text{(v)} \quad f_{\max} &= \frac{\text{slew Rate}}{2\pi V_p} \\ &= \frac{2\text{V}/\mu\text{s}}{2\pi (14)} \\ &= 22.74\text{kHz} \# \end{aligned}$$

(b) (i)

$$\begin{aligned} V_o &= -\left( \frac{R_f}{R_2} V_i + \frac{R_f}{R_1} V_i \right) \\ &= -R_f V_i \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \# \text{ shown} \end{aligned}$$

$$\begin{aligned} \text{(ii)} \quad V_o &= -(5.6\text{k}\Omega)(150\text{mV}) \left( \frac{1}{2.2\text{k}\Omega} + \frac{1}{2.9\text{k}\Omega} \right) \\ &= -0.597\text{V} \# \end{aligned}$$