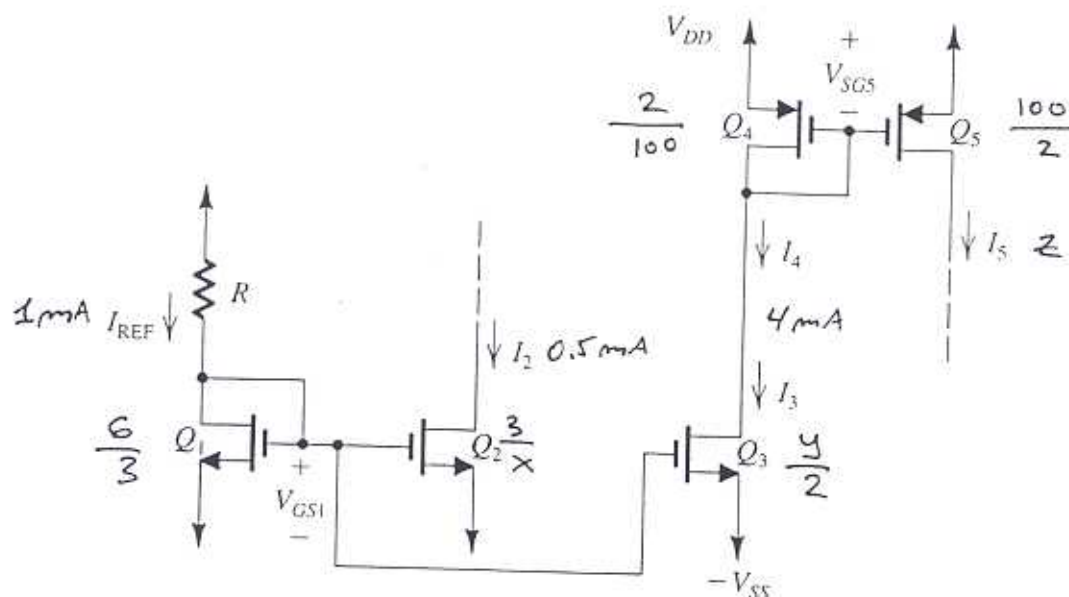


In the below schematic, $I_{REF}=1\text{ mA}$, $I_2=0.5\text{ mA}$, $I_3=I_4=4\text{ mA}$, W/L of $Q_1=6/3$, W/L of $Q_2=3/X$, W/L of $Q_3=Y/2$, W/L of $Q_4=2/100$, and W/L of $Q_5=100/2$. Showing your work, find X , Y , and I_5 .



$$\frac{\frac{3}{X}}{\frac{6}{3}} = \frac{0.5\text{ mA}}{1\text{ mA}} \quad , \quad X = 3$$

$$\frac{\frac{Y}{2}}{\frac{6}{3}} = \frac{4\text{ mA}}{1\text{ mA}} \quad , \quad Y = 16$$

$$\frac{\frac{100}{2}}{\frac{2}{100}} = \frac{I_5}{4\text{ mA}} \quad , \quad I_5 = 10\text{ A} !!!$$

(5pts) $X = 3$, (5pts) $Y = 16$, (5pts) $I_5 = 10\text{ A}$

NOTE: UNITS WERE
NOT SPECIFIED.
O.K. IF ~~PUT~~ PUT
" μm "

MUST INDICATE
UNITS

EG 2225

40

ECE 113B Midterm Exam
(February 12, 2004, Professor Kleinfelder)

CLOSED BOOK AND NOTES, NO ELECTRONIC AIDS
To receive credit, please show all work and place your answers where requested.

NAME: _____ ID: _____

Signature: _____ Seat/Row: _____

(5 pts) An n-channel transistor has $V_A=50V$, $V_t=1$, $V_{GS}=2$, $(W/L)=5$, and $k_n'=100\mu A/V^2$. Find r_o :

$$\begin{aligned} I_D &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 \\ &= \frac{1}{2} (100 \mu A/V^2) (5) (2-1)^2 = 250 \mu A \\ r_o &= V_A / I_D = 50V / 250 \mu A = 200 k\Omega \end{aligned}$$

(2 pts) What is the name of the phenomena that causes r_o ?

CHANNEL LENGTH MODULATION

(3 pts) What would r_o be if V_A were infinite?

INFINITE

(3 pts) What is the slope of the above transistors I-V curve when in saturation (include units)?

$$\frac{1}{r_o} = 5 \mu A/V \left(5 \times 10^{-6} A/V \right) \left(\frac{1}{200k} \right)$$

(5 pts) If the transistor's $\chi=0.1$, $v_{gs}=1V$, $v_{sb}=2V$, and its transconductance is $1mA/V$, find g_{mb} :


$$\begin{aligned} g_{mb} &= \chi g_m = (0.1)(1mA/V) \\ &= 0.1 mA/V \end{aligned}$$

(NOTE, V_{gs} , V_{sb} ARE IRRELEVANT HERE)

(2 pts) What phenomena is responsible in the above question?

BODY EFFECT

Refer to this figure for this page:

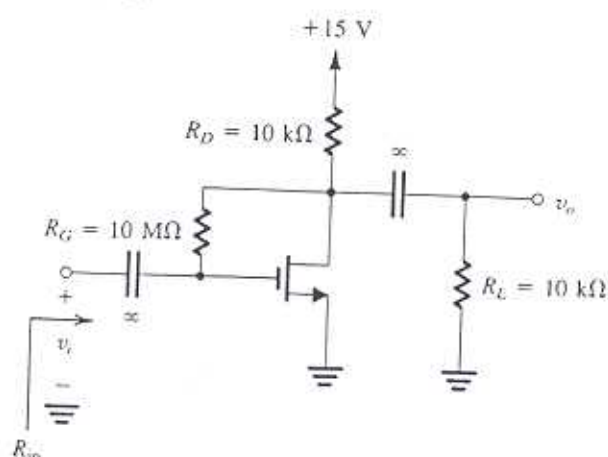

(2 pts) What kind of amplifier is this?


COMMON SOURCE AMPLIFIER

(3 pts) Explain the purpose of the resistor R_G :


PRIMARY: BIASES GATE VOLTAGE SUCH THAT Q IS IN SATURATION

SECONDARY: FEEDBACK STABILIZES I_D

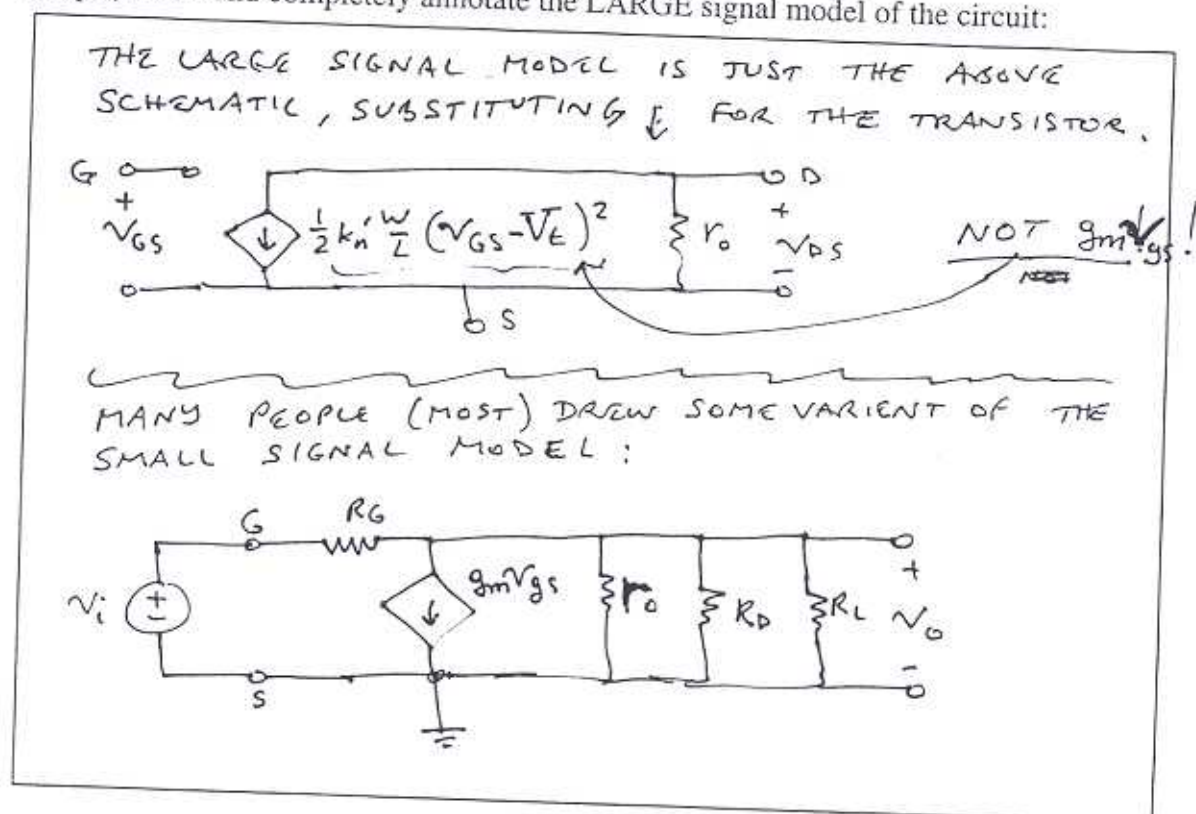(10 pts) Draw and completely annotate the LARGE signal model of the circuit:



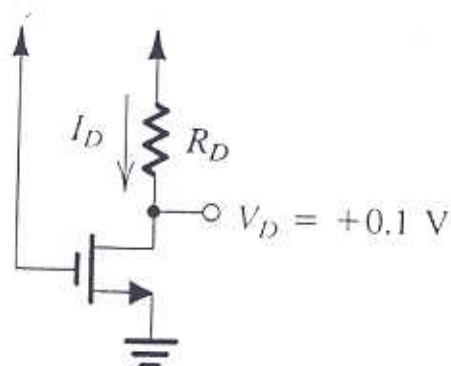Let the following NMOS transistor have a V_t of 1V, $\mu_n C_{ox} = 200 \mu A/V^2$, $\lambda = 0$, $L = 1 \mu m$, and $W = 10 \mu m$. Set $V_{dd} = 10V$.



(10 pts) Showing your work, find the I_D that will yield an V_D of 0.1V:

$$V_{DS} < V_{GS} - V_t \quad (0.1) < (10 - 1) \quad \checkmark \quad \text{TRIODE}$$

$$\begin{aligned} I_D &= k_n' \frac{W}{L} \left[(V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right] \\ &= (200 \mu A/V^2) (10) \left[(10 - 1)(0.1) - \frac{1}{2} (0.1)^2 \right] \\ &= 1.79 \text{ mA} \end{aligned}$$


ANSWER 1.79 mA

(5 pt) Find R_D :

$$E = IR \quad R = \frac{E}{I} = 5.53 \text{ k}\Omega$$

ANSWER 5,530 Ω (5.53 k Ω)

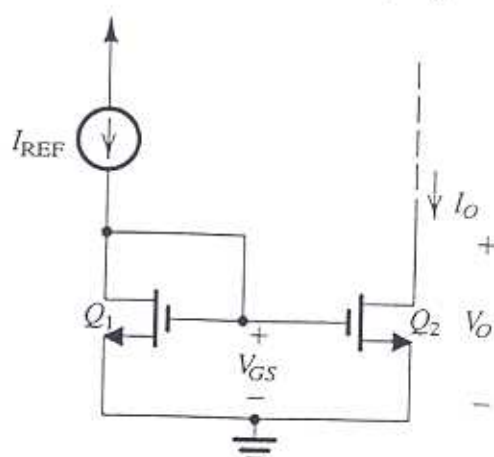In the following figure, let $I_{REF}=1\text{ mA}$, $L_2=L_1$, $W_2=2W_1$, $V_{GS}=2\text{ V}$, $V_O=4\text{ V}$, $V_{A2}=100\text{ V}$



CHANNEL-LENGTH MODULATION!

(10 pts) Find I_O :

$$\left(\text{SATURATION } I_O = I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS}) \right)$$

NO λ : $\frac{I_O}{I_{REF}} = \frac{(W/L)_2}{(W/L)_1}$, $I_O = \frac{(2)}{(1)} (1\text{ mA}) = 2\text{ mA}$


$$(1 + \lambda V_{DS2}) = (1 + V_O / V_{A2})$$

V_{A1} DOES NOT MATTER BECAUSE WE ARE GIVEN V_{GS} !

CH. LEN. MOD. WILL CHANGE I_O TO THE DEGREE THAT V_O DIFFERS FROM V_{GS} (V_{DS} OF Q_1), SO


ANSWER $I_O' = I_O \left(1 + \frac{V_O - V_{GS}}{V_{A2}} \right) = 2\text{ mA} \left(1 + \frac{4-2}{100} \right) = \underline{\underline{2.04\text{ mA}}}$

Refer to this figure for the next page

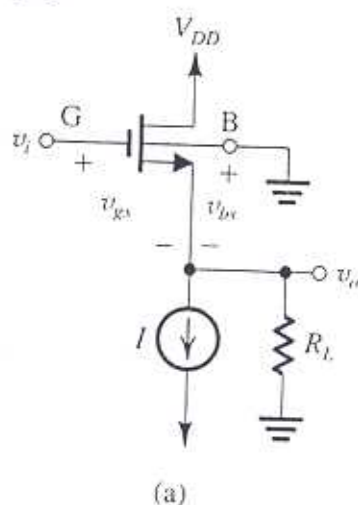


(~~scribbled out text~~)

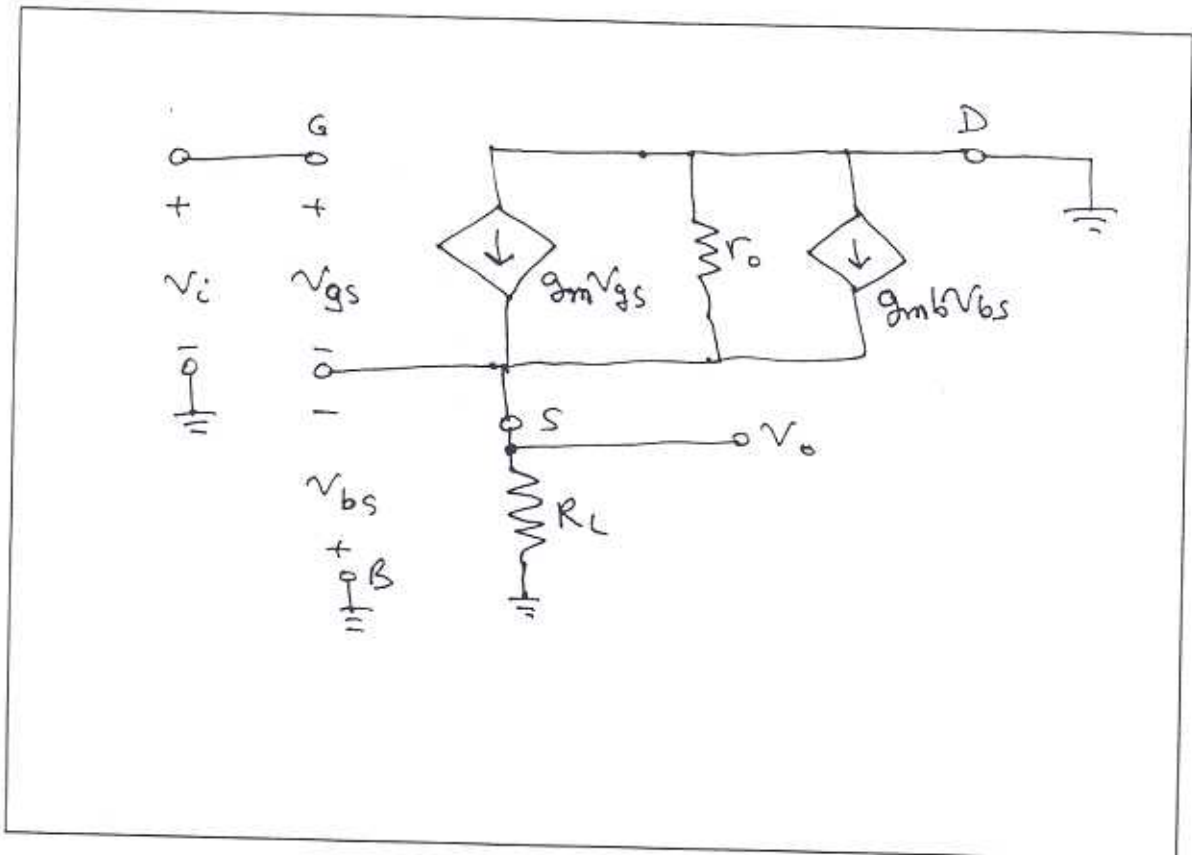(10 pts) Draw and annotate the complete SMALL signal model of this circuit:



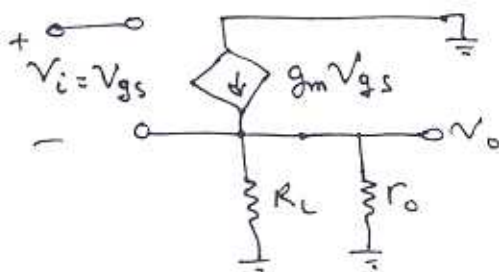(10 pts) Leave out any body effect, and derive the formula for the voltage gain of the entire circuit (including R_L) in terms of g_m , etc. Again, do not include the body effect:



$$v_o = g_m v_{gs} (R_L \parallel r_o)$$

NOTE: NON INVERTING!


$$A_V \equiv \frac{v_o}{v_i} = \frac{g_m v_{gs} (R_L \parallel r_o)}{v_i}$$

$$v_{gs} = v_i - v_o$$

$$v_i = v_{gs} + g_m v_{gs} (R_L \parallel r_o)$$

$$A_V = \frac{g_m v_{gs} (R_L \parallel r_o)}{1 v_{gs} + g_m v_{gs} (R_L \parallel r_o)} = \frac{g_m (R_L \parallel r_o)}{1 + g_m (R_L \parallel r_o)}$$
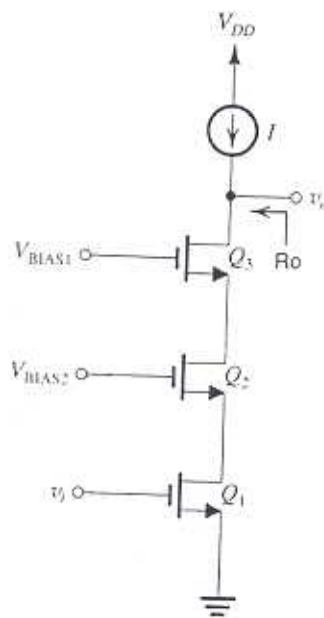
$$\text{ANSWER } A_V = \frac{g_m (R_L \parallel r_o)}{1 + g_m (R_L \parallel r_o)}$$



(5 pts) If all transistors in the above circuit have identical r_o and g_m , what is the output resistance R_o at the output of this circuit?

$$\begin{aligned}
 R_o &= (g_{m3} r_{o3})(g_{m2} r_{o2})(r_{o1}) \\
 &= g_m^2 r_o^3 \quad (= A^2 r_o)
 \end{aligned}
 \quad \left. \vphantom{\begin{aligned} R_o &= (g_{m3} r_{o3})(g_{m2} r_{o2})(r_{o1}) \\ &= g_m^2 r_o^3 \quad (= A^2 r_o) \end{aligned}} \right\} \begin{array}{l} \text{EITHER} \\ \text{IS FINE} \end{array}$$

ANSWER _____

Please report any problems you found in this exam below.

Thank you.